

ELEC 302 Lab 1

Xander Naumenko

05/02/24

1 Task 1

Part 1.

Part 2.

For the capacitor, we can use the formula given in class to calculate the value:

$$C = \frac{V_p - V_d}{f R_L V_r} = \frac{16.8 - 0.7}{60 \cdot 1000 \cdot 1} = 268.3 \mu\text{F}.$$

Since we don't have any capacitor values close to that, we instead used one $220 \mu\text{F}$ and two $33 \mu\text{F}$ capacitors in parallel which has an equivalent capacitance of $286 \mu\text{F}$.

2 Task 2

Part 1.

For the capacitor using the equation:

$$C = \frac{V_p - 2V_d}{2f R_L V_r} = \frac{33.2 - 1.4}{2 \cdot 60 \cdot 1000 \cdot 1} = 265 \mu\text{F}.$$

Again we used the same capacitor configuration as before of $286 \mu\text{F}$ since we didn't have a single capacitor of the correct value.

Part 2.

Again, the capacitor comes from the equation:

$$C = \frac{V_p - V_d}{2f R_L V_r} = \frac{16.8 - 0.7}{2 \cdot 60 \cdot 1000 \cdot 1} = 134 \mu\text{F}.$$

Three $33 \mu\text{F}$ capacitors were used in parallel to simulate this.